EE1118 Fundamental of Electrical and Electronic Engineering

Activity 4


Aim: Verify the load current using Thevenin Theorem **Date:**

Calculate:

(a) Thevenin equivalent voltage
(b) Thevenin equivalent resistance
(c) Load current.

Considering $R_1 = 10\ k\cap$, $R_2 = 10\ k\cap$ and $R_3 = 1\ k\cap$

Circuit Diagram

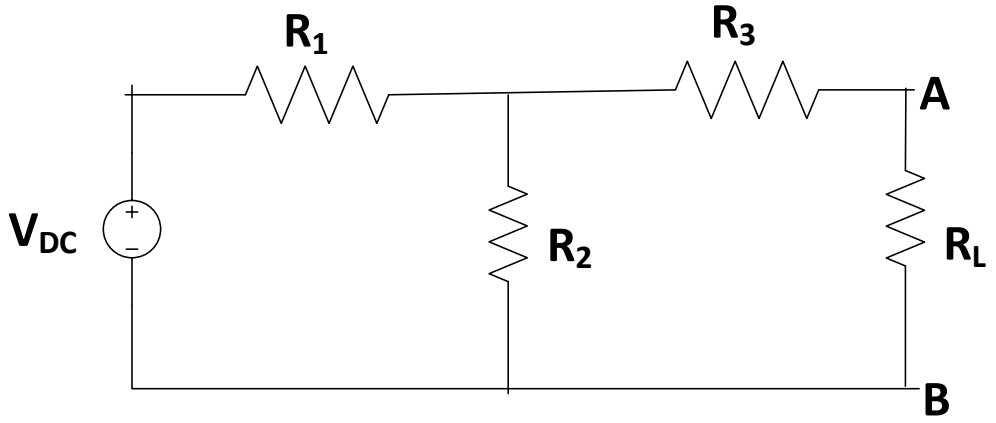

Observation Table

S. N.	Load Resistance	V_{th}	R_{th}	Load voltage (V_L)	Load Current (I_L)
1	2.5 $k\cap$				
2	5 $k\cap$				
3	7.5 $k\cap$				